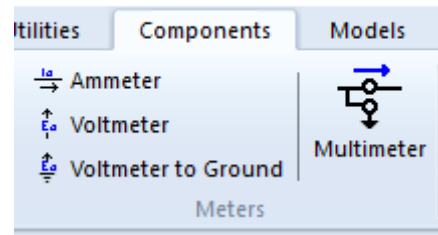




# Schematic






$I_a$

$E_a$

1.0 [ohm]

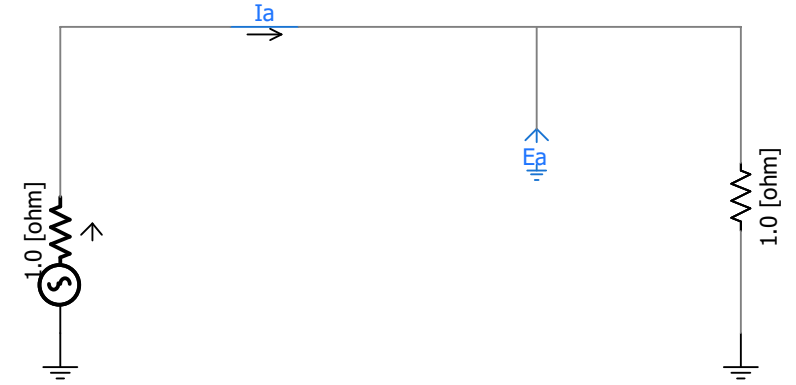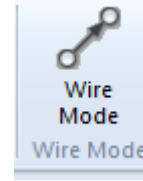




## SOURCES

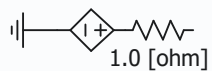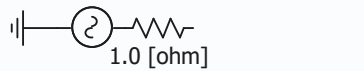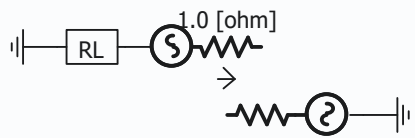

More on Sources



## PASSIVE ELEMENTS

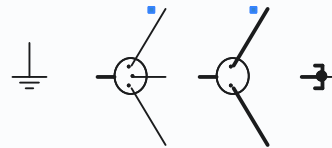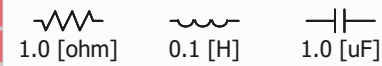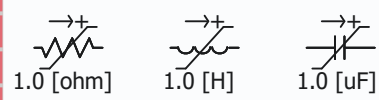

More on Passive Elements

